

Experiment # 1
Code Converters using MSI Components

1-Objective:

The aim of this experiment is to implement a Boolean Function using MSI components [Decoders, MUX's]


2- Equipment:

Type of IC	Description
74138	3×8 decoder
7432	OR Gate
74153	4×1 MUX
7404	Inverter

3- Procedure:

Part A: Implementation of a Full Adder with a decoder:

1- The function diagram is following :

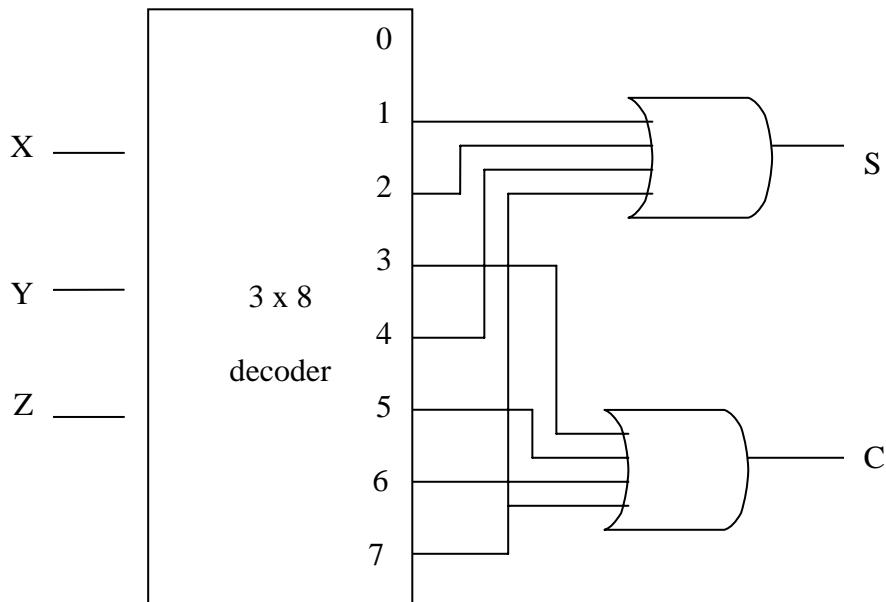

2- Derive the wiring diagram.

3- Connect the circuit given by the function diagram according to the derived wiring diagram.


4- Complete the truth table by measuring the outputs S, C.

x	y	z	c	s
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Part B: Implementation of a Boolean function using multiplexers

a- $F(A, B, C) = \sum\{1, 3, 5, 6\}$

1- The function diagram is following :

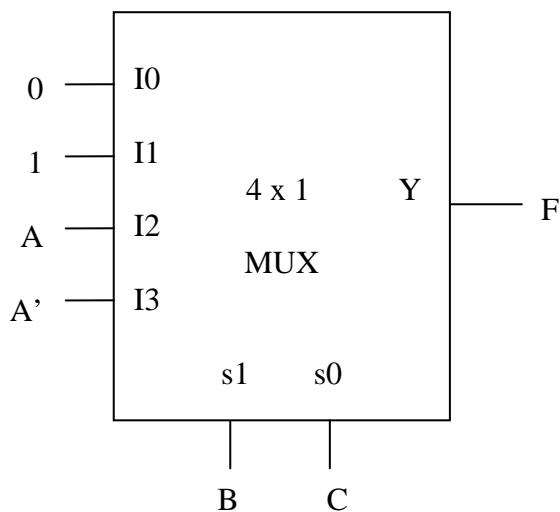

2- Derive the wiring diagram.

3- Connect the circuit given by the function diagram according to the derived wiring diagram.

4- Complete the table by measuring the output F.

A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

b- $F(A, B, C) = \sum\{1, 2, 4, 5\}$

1- Derive the function diagram.

2- Derive the wiring diagram.

3- Connect the circuit given by the function diagram according to the wiring diagram.

4- Complete the table by measuring the output F.

A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

4- Conclusions & Exercises:

1- Implement the following functions using 3×8 decoder:

$$F1(A, B, C) = \sum(2, 4, 7)$$

$$F2(A, B, C) = \sum(0, 3)$$

$$F3(A, B, C) = \sum(0, 2, 3, 4, 7)$$


2- Implement the following function using 4×1 MUX:

$$F(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$$


3- Write your conclusion about this experiment.

5 – Pin diagram:


Function: Hex INVERTER

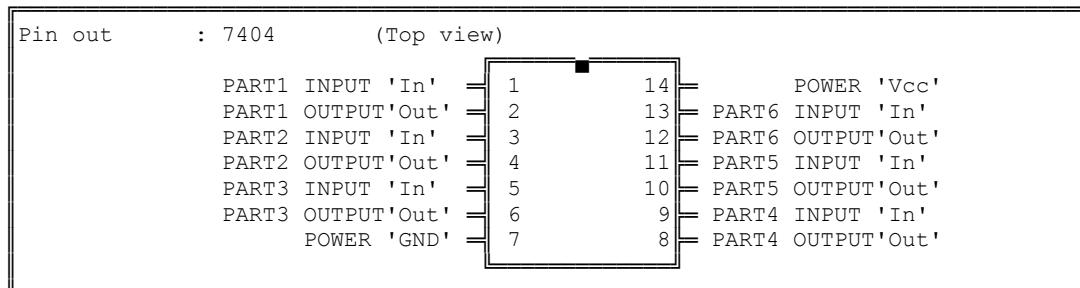

Function: Quad 2-input OR Gate

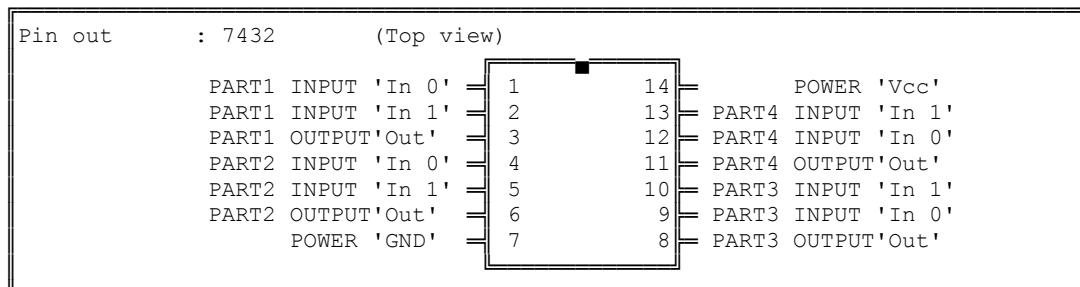

Function: 3-to-8 lines Decoder

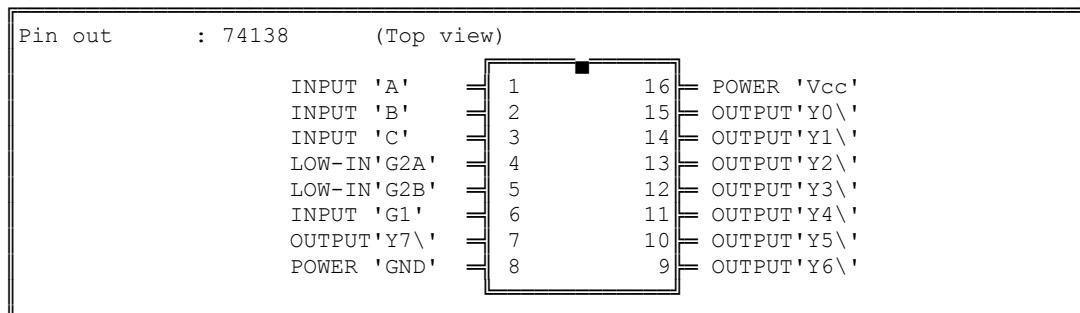

Function: 4x1 MULTIPLEXER

