

Experiment # 5
**Generation of control signals for serial
operation & serial transfer**

1-Objective:

The aim of this experiment is to generate control signals for serial operation and use them in serial addition .


2- Equipment:

Type of IC	Description
7490	Decade counter
7473	JK flip flop
7408	AND gate
74194	8 bit shift register

3- Procedure:

Part A: Generation of control signals for serial operation

1- The function diagram is following :

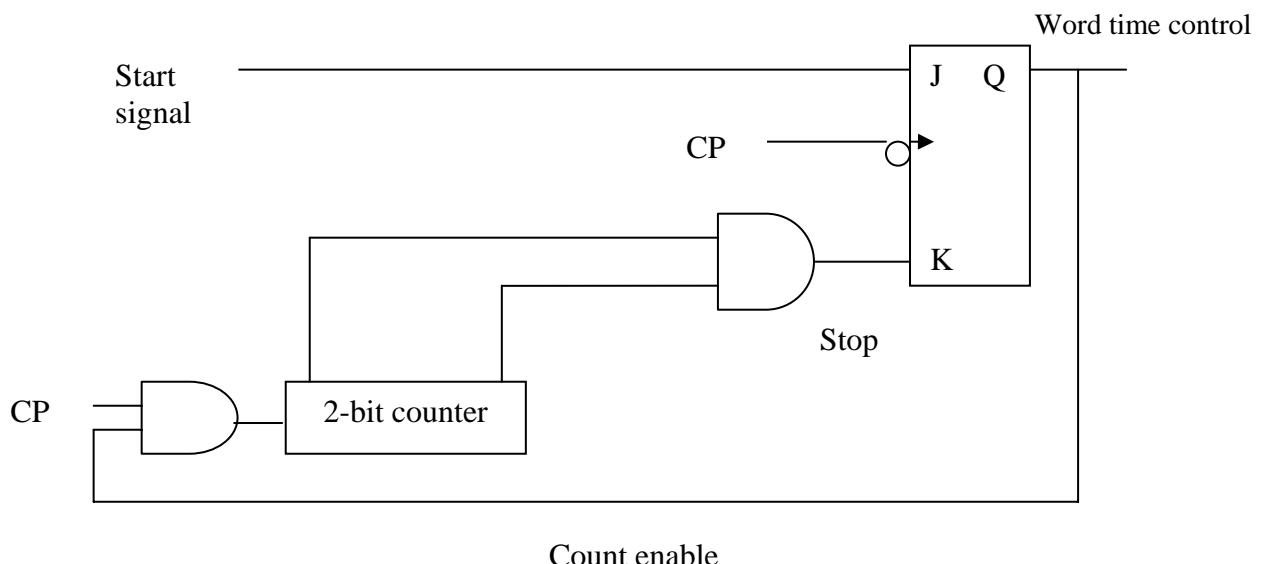

2- Derive the wiring diagram.


3- Connect the circuit given by the function diagram according to the derived wiring diagram.

4- Test the operation of the circuit.

5- Draw the circuit time waveforms.

Part B: Serial transfer

1- The function diagram is following :

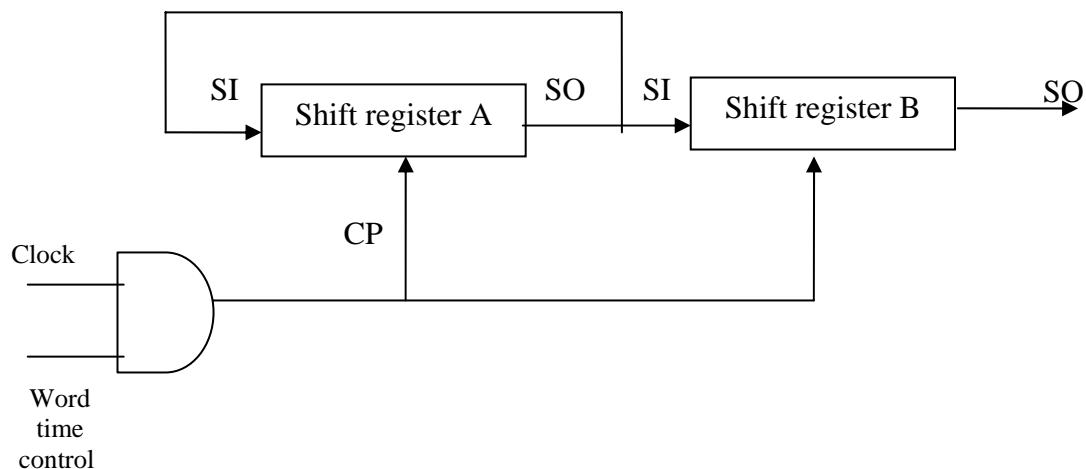

2- Derive the wiring diagram.

3- Connect the circuit given by the function diagram according to the derived wiring diagram.

4- Test the operation of the circuit.


6- Conclusions and Exercises

1- If registers A and B have 8 bits , generate a control signal for serial operation ?


2- Write your Conclusions about the experiment.

Data sheet


Function : 2-input-AND Gate

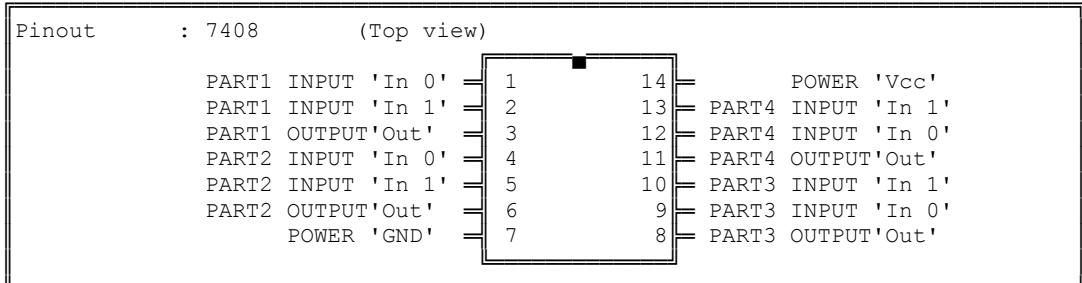

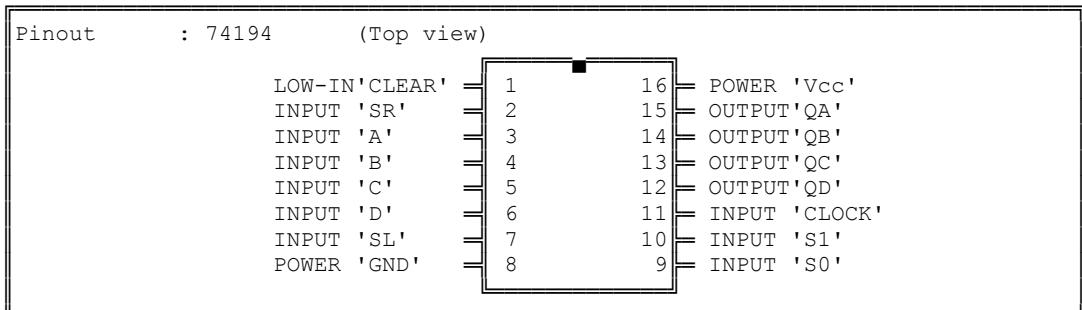Function : 4 Bit universal bidirectional shift register



Function : Decade counter

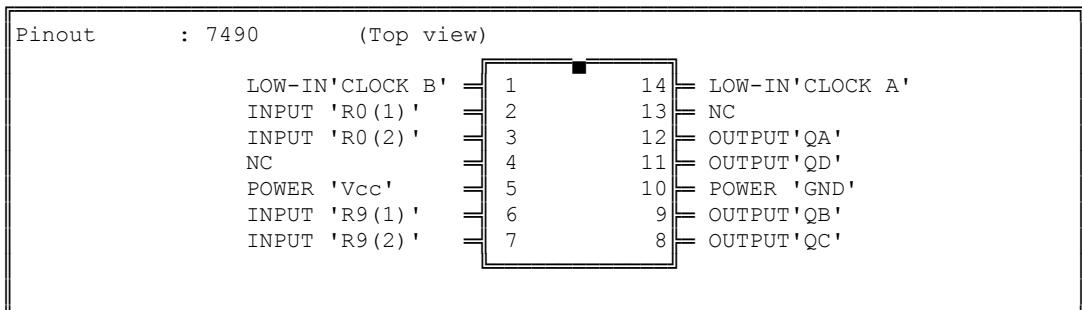

Function : J-K FLIPFLOP

